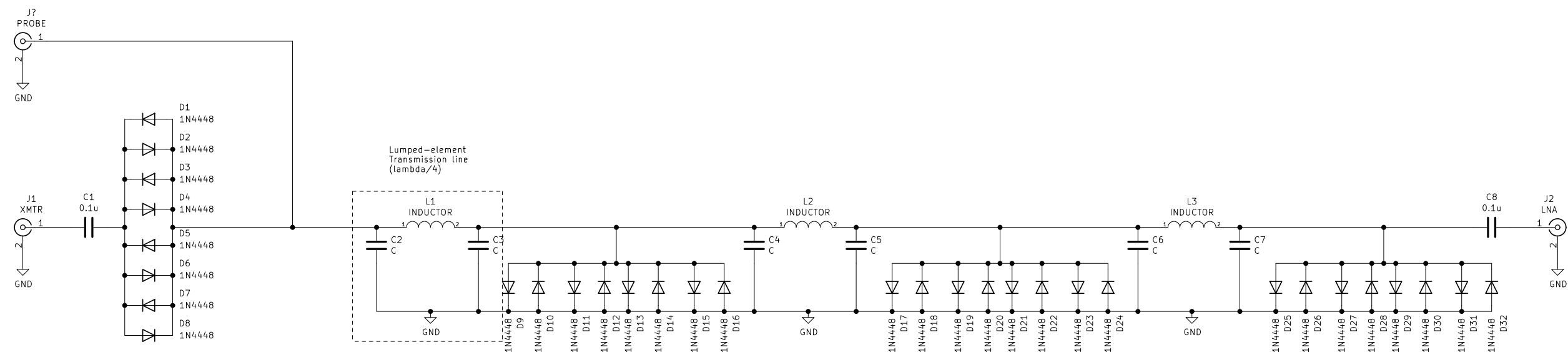


Passive transmit/recieve circuit with 3 stage lambda quarters (~10–350 MHz)



Equations (lambda/4)

$$C = \frac{1}{(\omega Z) \sin(\theta) / (1 + \cos(\theta))} = \frac{1}{(\omega Z) 20}$$
$$L = \frac{(Z / \omega) \sin(\theta)}{20} = \frac{20}{(\omega)}$$

0.585 T 1H (25.07 MHz)
C=127 pF
L=317 nH

Housing (box) [Not spacioius enough for 3 stages]
- Hammond Manufacturing 1590A (Digikey= HM150-ND)
- Hammond Manufacturing 1590B (Digikey= HM151-ND)
- Hammond Manufacturing 1590BFL (Digikey= HM572-ND)

- BNC Panel connector Amphenol 112639 (ACX2300-ND)

Non-magnetic component vendors

** Trimmers**

- Knowles Voltronics
- Voltronics
- EW Electronics (Sprague-Goodman) [SGC3 Series]

Fixed

- ATC
- PPI
- Johanson
- Syfer [C0G/NP0 (1B), High Q, X7R (2R1)]

Notes:

- There is a practical margin for lumped element values error when realizing the transmission line (pi-network).
- Check S parameters (S11, S21) of lumped transmission line prior to assembly, phase= -90 deg with reflection < -15 dB.
- Two stage lambda/4 may be sufficient to provide enough isolation between XTMR and LNA
- The design is adapted from the passive broadband T/R switch in the Varian spectrometer.